

Electrical Circuits

Application



Q1: How can we define a generator?

**A device that
provides an
electric current**


**A device that
receives an electric
current**



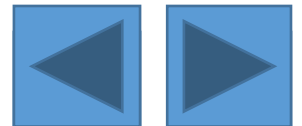Q2: How can we define a receiver?

**A device that
receives an
electric current**

**A device that
provides an
electric
current**



Q3: What is the dry cell?

Receiver


**Generato
r**



Q4: what is the lamp?

receiver


Generator
r

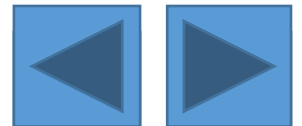

Q5: what is the motor?

Gnerator


receiver

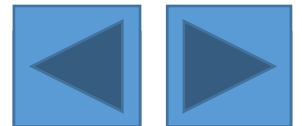

**Q6: what do we use to
connect a lamp to a
generator?**

Wires


Switch

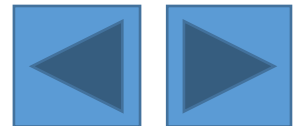

**Q7: when does the lamp
shine in a circuit?**

**When the
switch is
open**


**When the
switch is
closed**

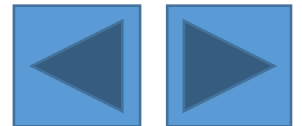

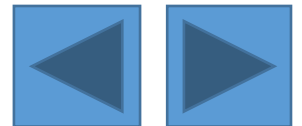Q8: when the circuit is said to be opened?

**If there is no
passage of
electric
current**

**If there is
passage of
electric
current**



Q9: how many poles does the lamp have?

2

1



Q9: how many poles does the dry cell have?

1

2



Q1: How can we define a conductor?

**A body that
allows the
passage of an
electric current**

**A body that doesn't
allow the passage
of an electric
current**



Q2: How can we define an insulator?

**A body that
doesn't allow
the passage of
an electric
current**


**A body that
allows the
passage of an
electric
current**



Q3: What is the wood?

Conductor


Insulator

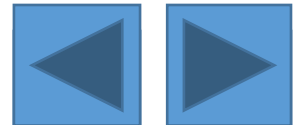

Q4: what is the aluminum?

Insulator


**Conducto
r**

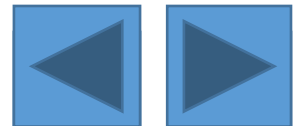

Q5: what is the paper?

Conductor


Insulator

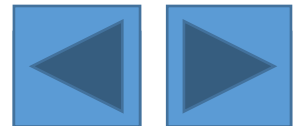

Q6: what is human body?

Conductor

Insulator

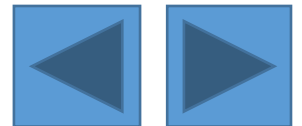


Watch this video about the types of an electric circuit:




**Q7: what are the two
types of electric circuit?**

**Conductor
and
insulator**


**Series and
parallel**

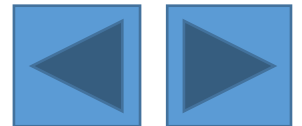

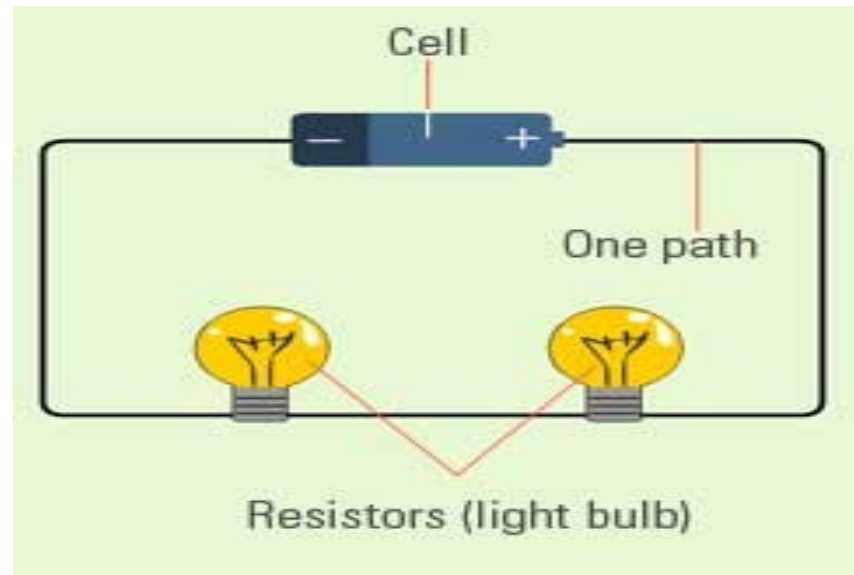A series circuit is one that has more than one lamp, but only one path through which the electricity flows. From one end of the dry cell (battery), the current moves along one path with NO branches.



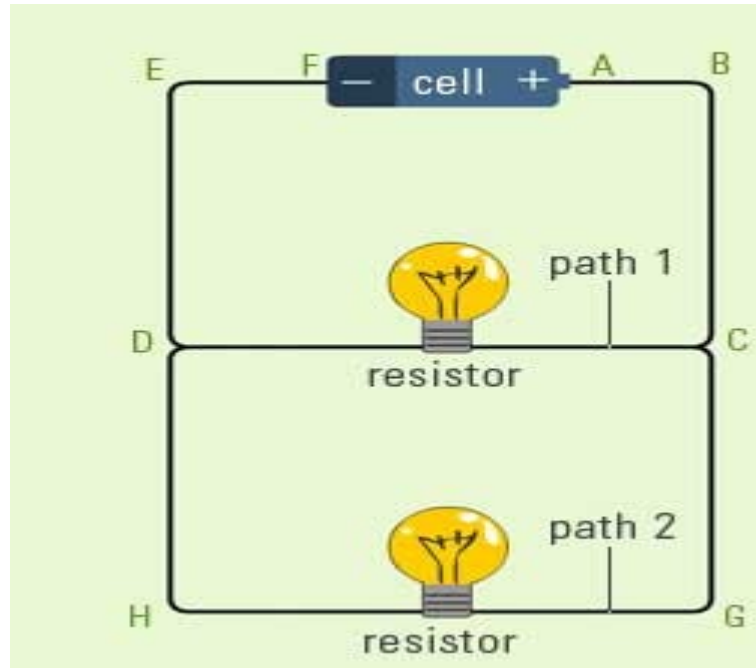In a parallel circuit, there is more than one lamp and they are arranged on many paths. This means that electricity can travel from one end of the cell through many branches to the other end of the cell.




**Q8: How many branches
does the series circuit
have?**

1

Many



Q9: this circuit is series or parallel?

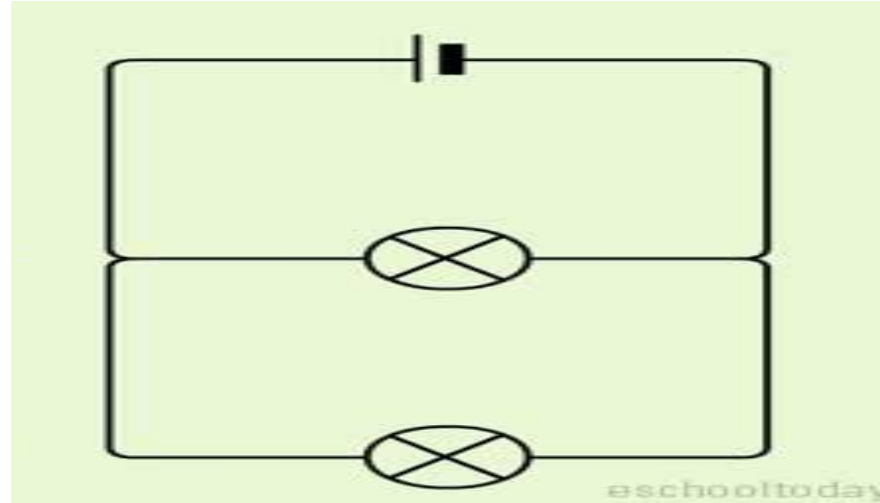


Parallel

Series



Q10: this circuit is series or parallel?

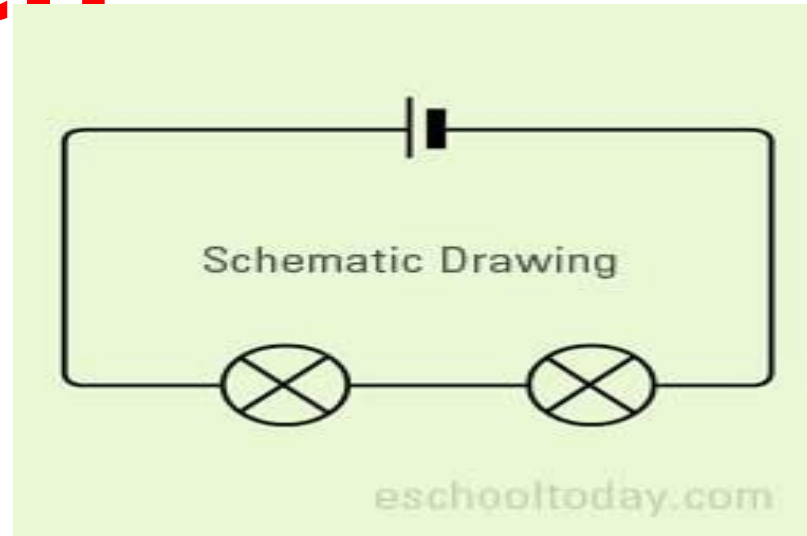

Series

Parallel



The END

